
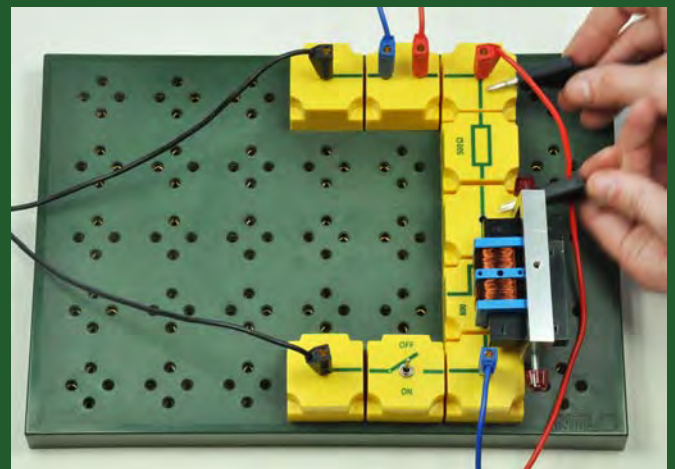


Student Experiments

Manual

ELECTROMAGNETISM

P9160-4P

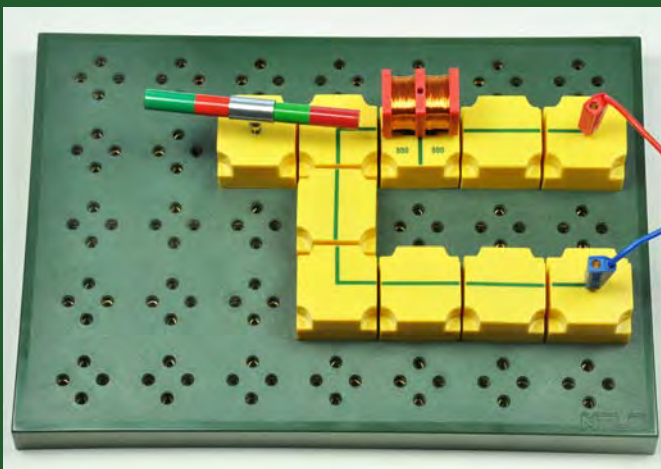

INDEX

3. THERMAL ENERGY DERIVED FROM ELECTRICAL ENERGY

- ELS 3.6 Bimetal fuse
- ELS 3.7 Bimetallic thermostat
- ELS 3.8 Bimetallic fire alarm

4. WORK AND POWER

- ELS 4.1.1 The power of an electric motor

6. ELECTROMAGNETISM

- ELS 6.1 Electrical current generates a magnetic field
- ELS 6.2 The magnetic field of a coil
- ELS 6.3 A magnetically manipulated switch
- ELS 6.4 A relay
- ELS 6.5 Relay with operating point and normal contact
- ELS 6.6 Self-opening switches
- ELS 6.7 An AC buzzer
- ELS 6.8 Model of a magnetic fuse

7. KINETIC ENERGY DERIVED FROM ELECTRIC ENERGY

- ELS 7.1 Motoric effects of electricity
 - ELS 7.1.1 Lorentz' force
- ELS 7.2 Principle of the electric motor
- ELS 7.3 Model of the electric motor
 - ELS 7.3.1 Direct current motor
- ELS 7.4 Wound series electric motor
- ELS 7.5 Shunt-wound motor
- ELS 7.6 Model of a moving iron measuring instrument


8. ELECTROMAGNETIC INDUCTION

- ELS 8.1 Induction
 - ELS 8.1.1 Induced electromotive force
- ELS 8.2 Principle of a generator
- ELS 8.3 The AC generator (internal pole generator)
- ELS 8.4 The AC generator (external pole generator)
- ELS 8.5 The DC-generator
- ELS 8.6 Generators with electromagnets
 - ELS 8.6.1 Internal pole generator with electromagnet
- ELS 8.7 Induction by DC
- ELS 8.8 Transformer
 - ELS 8.9 Transformer 1:1
 - ELS 8.10 Unloaded transformer
 - ELS 8.11 The current intensity is transformed as well
 - ELS 8.12 Coils connected to DC
 - ELS 8.13 Cut out peaks due to self-induction
 - ELS 8.13.1 Lenz' Law
 - ELS 8.13.2 Braking effect due to self-induction
 - ELS 8.14 Coils connected to AC
 - ELS 8.15 AC resistance of a coil
 - ELS 8.16 Resistance and inductance in AC

Required Kit:

P9901-4D Electricity 1

P9902-5P Electromagnetism

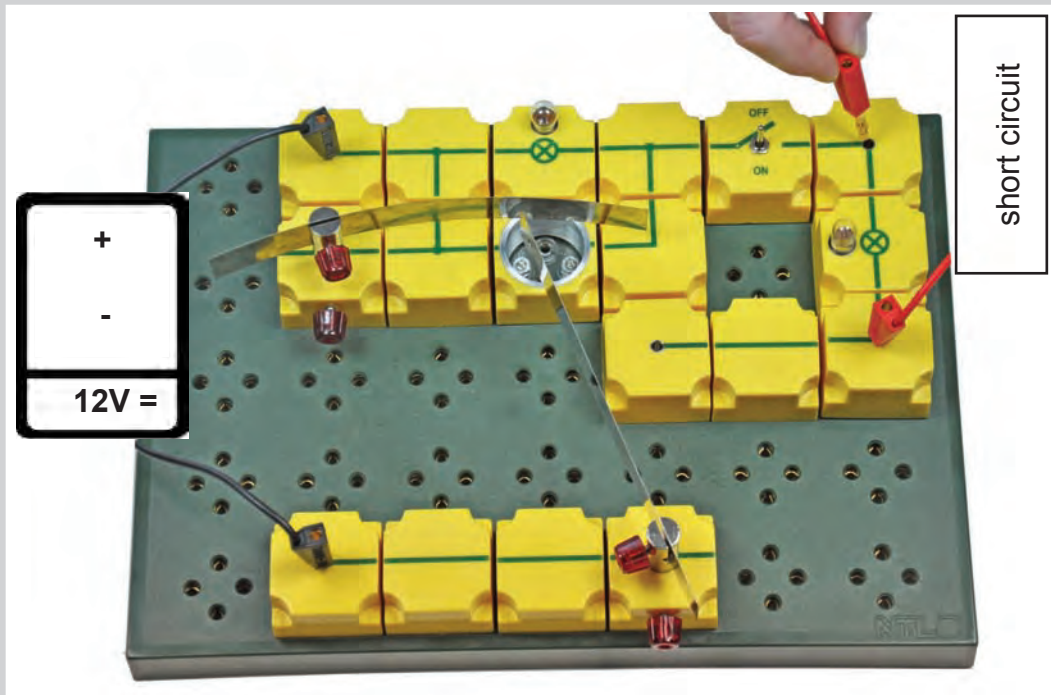

Material:

- 1x Plug-in panel
- 2x Connecting lead, black
- 1x Connecting lead, red
- 3x PIB connector
- 3x PIB wire, straight
- 3x PIB wire, T-shaped
- 2x PIB wire, angled, with socket
- 1x PIB wire, angled
- 1x PIB switch, ON/OFF
- 2x PIB with adapter bush
- 2x PIB lamp socket, E10
- 2x Light bulb, 10V/50mA, E10
- 2x Holder with slit and hole
- 1x PIB with heating coil
- 1x Bimetallic strip
- 1x Flat spring, steel, 0.2mm

Additionally required:

- 1x Voltage supply

In einer automatischen Sicherung kann eine Bimetallsicherung als Schutz gegen Überlastung vorhanden sein.

Wiring:

Arrangement of the wiring according to the illustration.


After inserting all plug-in blocks in the circuit board the following arrangements are to be made very carefully:

The flat spring has its neutral position in the position marked by hatching.

Its distance to the crocodile clip with plug pins inserted in A is about 5 mm.

The bimetallic strip outside (patterened side pointed to the front) is moved from the left side towards the end of the flat spring exactly above the heating spiral.

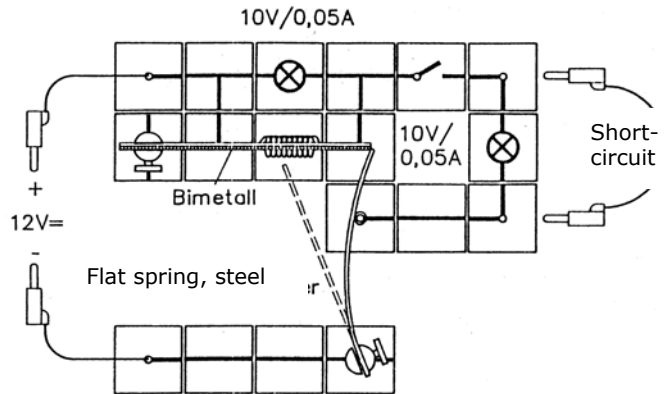It slightly presses against the crocodile clip with plug pin at A. 12 V DC is applied.



Experiment:

The switch is closed.

The circuit is closed because the flat spring contacts the crocodile clip at A and the right lamp glows.

The upper lamp connected in parallel with the heating spiral does not yet glow.

The right lamp is short-circuited.

Now the upper lamp indicates a voltage through the heating spiral which causes it to glow.

After a short while the bimetallic strip bends and releases the end of the flat spring.

The flat spring springs back to its neutral position, thus the circuit is interrupted.




Conclusion:

A bimetallic strip connected in a certain way may interrupt a circuit because of being heated.

Advice:

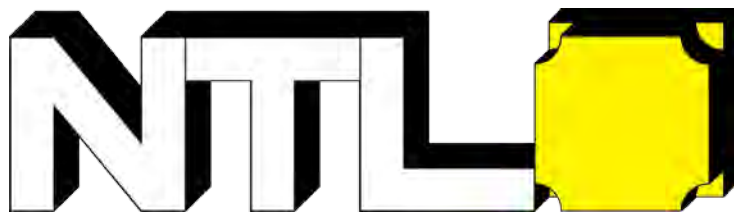1. How long it takes for the disconnection to occur depends on the setup.
2. If no lamp is glowing before the disconnection occurs there is no contact at A.





Student Experiments

© Fruhmann GmbH
NTL Manufacturer & Wholesaler

Werner von Siemensstraße 1
A - 7343 Neutal
Austria

www.ntl.at